


Logic Gates

ISHITA KANODIA

→ a digital circuit following boolean algebraic expressions.

I OR Gate

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 

II AND Gate

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1




III NOT Gate

A	Y
0	1
1	0




NAND (AND + NOT)

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 

IV NOR gate (OR + NOT)


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

 

ISHITA KANODIA


VI NOT from NAND

A	B = (A)	Y
0	0	1
1	1	0

 


VII AND from NAND

A	B	Y'	Y
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

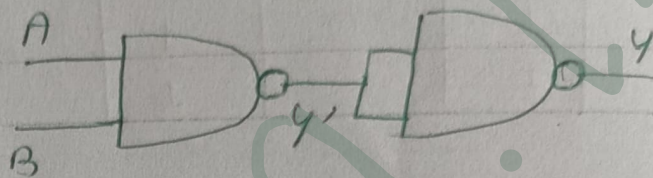


VIII OR from NAND

A	B	$\bar{A}$	$\bar{B}$	Y
0	0	1	1	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	1

 


IX NOT from NOR


A	B = (A)	Y
0	0	1
1	1	0

 

X AND from NOR

 

XI OR from NOR

 

Boolean Algebra

OR	AND	NOT
$A+0 = A$	$A \cdot 0 = 0$	$A+\bar{A} = 1$
$A+1 = 1$	$A \cdot 1 = A$	$A \cdot \bar{A} = 0$
$A+A = A$	$A \cdot A = A$	$\bar{\bar{A}} = A$

$$\rightarrow A + AB = A$$

$$\rightarrow A \cdot (A+B) = A$$

$$\rightarrow A + (\bar{A}B) = A+B$$

$$\rightarrow A \cdot (\bar{A} + B) = A \cdot B$$

$$\rightarrow A + (B \cdot C) = (A+B) \cdot (A+C)$$

$$\rightarrow (\bar{A} + B) \cdot (A + C) = \bar{A} \cdot C + B \cdot A + B \cdot C$$

De Morgan's Theorems

$$\text{1st Theorem} \Rightarrow \overline{A+B} = \bar{A} \cdot \bar{B}$$

$$\text{2nd Theorem} \Rightarrow \overline{A \cdot B} = \bar{A} + \bar{B}$$