

1.

Current Electricity
The rate of flow of charge across any cross-section is called electric current.

$$I = \frac{dq}{dt}$$

2. Current density is the current flowing per unit area through any cross-section.

$$J = \frac{I}{A}$$

$$I = \vec{J} \cdot \vec{A} = JA \cos \theta$$

(direction of $\vec{J}$ = direction of I).

3. Drift velocity is the avg. velocity with which e^- s get drifted from low potential to high potential of a conductor.
(+ve terminal) (-ve terminal)

$$V_d = az = -\frac{eE}{m} \tau$$

$$I = neAV_d$$

$$J = neV_d$$

$$\mu = \text{mobility} = \frac{V_d}{E} = \frac{e\tau}{m}$$

→ When no external electric field is applied $\Rightarrow$ avg. thermal vel. = 0
avg. thermal speed $\neq 0$.

$$\frac{1}{2} m V_{rms}^2 = \frac{3}{2} kT$$

→ $\lambda = \text{mean free path} = \frac{\text{total distance travelled}}{\text{no. of collisions}} = \text{distance between 2 successive collisions}$

→ $\tau = \text{relaxation time} = \frac{\text{total time between 2 collisions for all } e^-}{\text{no. of } e^-}$

4. $J = neV_d = \sigma E \Rightarrow$ Ohm's law at microscopic level.

$$\sigma = \text{conductivity} = \frac{ne^2\tau}{m} \quad V = IR \quad R = \frac{\rho l}{A}$$

$$\rho = \text{resistivity} = \frac{1}{\sigma} = \frac{m}{ne^2\tau}$$

→ Thus, according to Ohm's law, the current flowing through a conductor is directly proportional to the potential difference across the ends of the conductor, provided that the physical state (T, P) of the conductor remains constant.






5. α = ^{temp.} coefficient of resistance / resistivity.

→ For conductors $\alpha = +ve \Rightarrow \text{Temp. } \uparrow \Rightarrow z \downarrow \Rightarrow \rho \uparrow \Rightarrow R \uparrow$
 For semiconductors, insulators $\alpha = -ve \Rightarrow \text{Temp. } \uparrow \Rightarrow \text{bonds break}$
 $\therefore n \uparrow \Rightarrow \rho \downarrow \Rightarrow R \downarrow$.

$$\rho_t = \rho_0 (1 + \alpha T)$$

$$R_t = \left[R_0 \left(1 + \int_{T_0}^T \alpha dT \right) \right] = R_0 (1 + \alpha T)$$

6. I-V characteristics

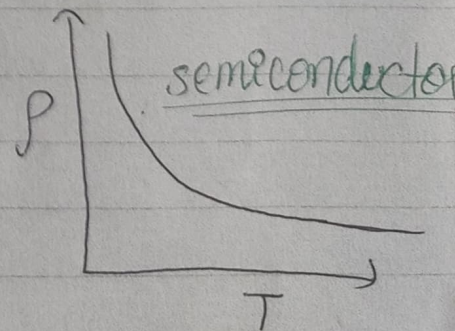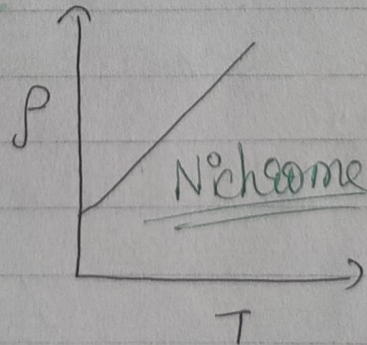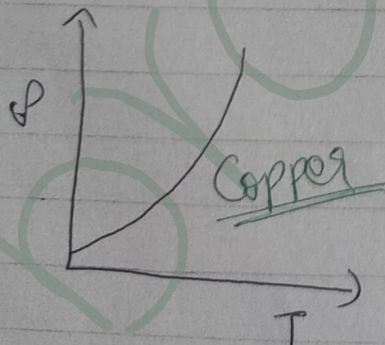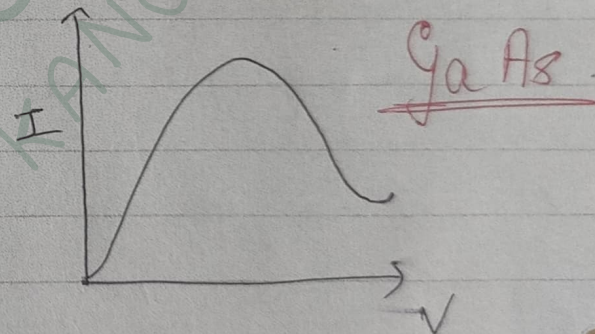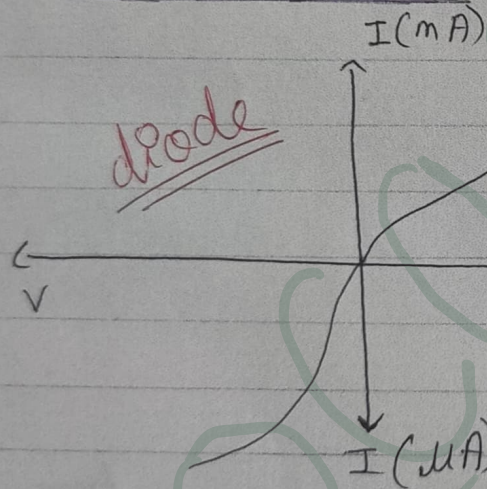

Combination -

Series - $R = R_1 + R_2 + \dots$

$$V = V_1 + V_2 + \dots$$

$I = \text{same}$

Parallel - $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$

$$I = I_1 + I_2 + \dots$$


$V = \text{same}$

8. Kirchhoff's Law - (1) Junction law - based on conservation of charge.

(2) Loop law - based on conservation of energy.

→ Symmetry -

(a) Path symmetry -

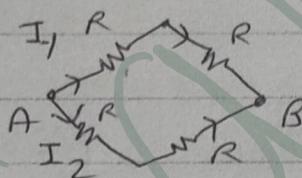

$$\underline{I_1 = I_2}$$

(b) $\perp^r$ axis symmetry -

- All points lying on the same line of symmetry have same potential. (Line of symmetry = equipotential line).
- All resistances on the line of symmetry can be removed.
- point of symmetry = false junction
 $\therefore$ remove the junction.

(c) Infinite Ladder - leave one unit $\Rightarrow$ take rest as x .
($R_{eq} \approx x$.)

9. Cell

(a) EMF $\Rightarrow$ The potential difference across the electrodes of the cell when no current is being drawn from the cell.

(b) Internal resistance (r) $\Rightarrow$ The opposition ^{to the} of flow of current inside the cell.

- distance between electrodes $\uparrow \Rightarrow r \uparrow$
- area of electrodes $\uparrow \Rightarrow r \downarrow$
- conc. of electrolyte $\uparrow \Rightarrow r \uparrow$
- temp. $\uparrow \Rightarrow r \downarrow$.

→ Series - $E = E_1 + E_2 + E_3 + \dots$
 $r = r_1 + r_2 + \dots$

$$E_{eq} = nE$$

$$r_{eq} = nr$$

$$I = \frac{nE}{nr + R_{eq}}$$

→ Parallel - $E_{eq} = \frac{E_1}{\frac{1}{r_1} + \frac{1}{r_2} + \dots}$

$$r_{eq} = \frac{1}{\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} + \dots}$$

$$E_{eq} = E$$

$$r_{eq} = \frac{r}{m}$$

→ Mixed - n columns (series) (total cells = $m \times n$)
 - m rows (parallel).

$$E_{eq} = nE$$

$$r_{eq} = \frac{nr}{m}$$

$$I = \frac{nE}{R_{eq} + \frac{nr}{m}}$$

- Current in the circuit is maximum when external resistance (R_{eq}) = total internal resistance.

$$R_{eq} = \frac{nr}{m}$$

→ Open circuit - $R = \infty$, $I = 0$ $V = E$

Short circuit - $R = 0$, $I = \frac{E}{r + R} = \frac{E}{r}$ $V = 0$

10. For balanced Wheatstone - $\frac{P}{Q} = \frac{R}{S}$ or $\frac{R_1}{R_2} = \frac{R_3}{R_4}$

- when $\frac{R_1}{R_2} < \frac{R_3}{R_4} \Rightarrow I$ from top to bottom

- when $\frac{R_1}{R_2} > \frac{R_3}{R_4} \Rightarrow I$ from bottom to top.

1. Meter bridge

For zero deflection ($I_g = 0$) / balanced condition

$$\frac{l}{100-l} = \frac{R}{S} \Rightarrow \frac{l}{(100-l)} = \frac{R}{S}$$

12. Potentiometer - It is a linear conductor of uniform cross-section with a steady current set up in it.
- uniform potential gradient $X = \frac{V}{l}$

(any potential difference which is less than the potential difference across the potentiometer wire can be measured.)

- Ideal voltmeter


- Applications - (i) comparison of emf of two cells
(ii) internal resistance of a given primary cell
(iii) comparison of two resistances.

13. Galvanometer - an instrument used to measure the strength of current by measuring the deflection of the coil due to torque acting on it produced by a magnetic field.

$$I \propto \theta$$

$$I = K\theta$$

(K = figure of merit of galvanometer)

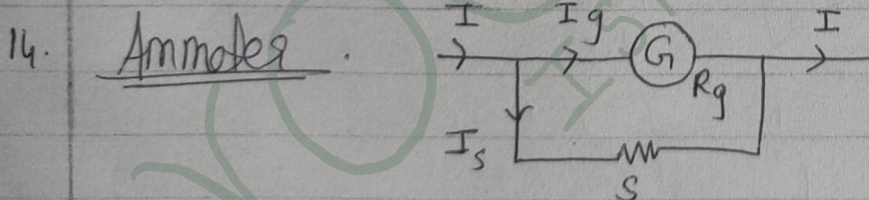


$$I = I_g + I_s$$

$$S = \frac{I_g R_g}{I - I_g}$$

S = shunt resistance (small)
 I = max. current that can be measured by the ammeter.

I_g = max. current that can flow through the galvanometer

Ideal ammeter has zero resistance.

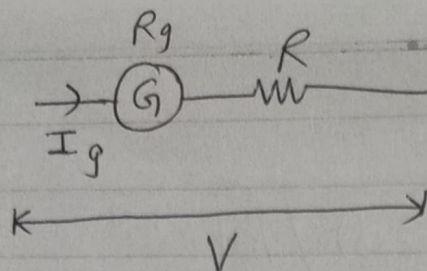15. Voltmeter -

$$R = \frac{V}{I_g} - R_g$$

$$R \rightarrow \infty$$

for ideal voltmeter.

16. Power - If current enters the high potential point of the device, then power is consumed by it. (load).
 - If current enters the low potential point of the device, then power is supplied by it. (source).

$$P = VI = I^2 R = \frac{V^2}{R}$$

17. Heating effect - When current passes through a resistor, energy is wasted in overcoming the resistance of the wire. This energy is converted into heat.

$$H = \int P dt = I^2 R t = \frac{V^2 t}{R} = VI t$$

$$\left(\begin{array}{l} 1 \text{ cal} = 4.2 \text{ J} \\ 1 \text{ J} = 10^7 \text{ erg} \end{array} \right)$$

$$H = \int_0^t I^2 R dt \Rightarrow \text{for variable } I$$

→ One unit of electrical energy = 1 kilowatt hour = 1 kWh
 $= 3.6 \times 10^6 \text{ J}$

18. Bulbs - series $\Rightarrow \frac{1}{P} = \frac{1}{P_1} + \frac{1}{P_2} + \dots$

parallel $\Rightarrow P = P_1 + P_2 + \dots$

$$\rightarrow R_{\text{bulb}} = \frac{V_{\text{rated}}^2}{P_{\text{rated}}}$$

→ brightness of bulb $\propto$ Power consumed by the bulb.

1. To convert voltmeter of $R_g \Omega$ and range V volts into a voltmeter of range nV volts, the value of resistance to be connected in series - $R = (n-1)R_g \Omega$

To convert ammeter of $R_g \Omega$ and range $I A$ into ammeter of range $nI A$, value of resistance to be connected in parallel - $R = \frac{R_g \Omega}{(n-1)}$

2. For two identical heater coils -
heat generated (H) -
(P = Parallel)
(S = series)

$$\frac{H_P}{H_S} = 4$$

$$T_S = T_1 + T_2$$

$$T_P = \frac{T_1 T_2}{T_1 + T_2}$$

NCERT Points

1. Commercially produced resistors for domestic use or in laboratories are of two major types: wire bound resistors and carbon resistors.

Carbon Coding

Colour	Number	Multiplier	Tolerance (%)	4 bands
Black	0	10^0		B
Brown	1	10^1		B
Red	2	10^2		} Roy
Orange	3	10^3		
Yellow	4	10^4		
Green	5	10^5		
Blue	6	10^6		} Great Britain and Victor
Violet	7	10^7		
Gray	8	10^8		
White	9	10^9		} were good souls.
Gold		10^{-1}	5	
Silver		10^{-2}	10	
No colour			20	

3. Junction rule: At any junction, the sum of the currents entering the junction is equal to the sum of the currents leaving the junction.

Loop rule: The algebraic sum of changes in potential around any closed loop involving resistors and cells in the loop is zero.

4. Jockey is essentially a metallic rod whose one end has a knife-edge which can slide over the wire to make electrical connection.